


### 交流回路の過渡現象

#### ・RL直列回路

$$\text{電源電圧 } v(t) = V_m \sin(\omega t + \theta)$$

回路方程式
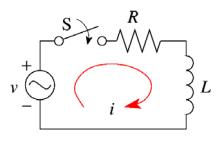
$$L \frac{di}{dt} + Ri = V_m \sin(\omega t + \theta)$$



・定常解 (交流理論より)

$$j\omega L I_s + RI_s = V_e e^{j\theta} \longrightarrow I_s = \frac{V_e e^{j\theta}}{R + j\omega L} = \frac{V_e}{\sqrt{R^2 + \omega^2 L^2}} e^{j(\theta - \phi)}$$

$\left( V_e = \frac{V_m}{\sqrt{2}}, \phi = \tan^{-1} \frac{\omega L}{R} \right)$

よって

$$i_s = I_m \sin(\omega t + \theta - \phi) \quad \left( I_m = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \right)$$

・過渡解

$$L \frac{di_t}{dt} + Ri_t = 0 \longrightarrow i_t = A e^{-t/\tau} \quad \left( \text{時定数 } \tau = \frac{L}{R} \right)$$

### 一般解

$$i = i_t + i_s = A e^{-t/\tau} + I_m \sin(\omega t + \theta - \phi)$$

初期条件  $t = 0 \Rightarrow i = 0$

$$A + I_m \sin(\theta - \phi) = 0 \longrightarrow A = -I_m \sin(\theta - \phi)$$

よって

$$i = I_m \sin(\omega t + \theta - \phi) - I_m \sin(\theta - \phi) e^{-t/\tau}$$


$$\text{ただし } I_m = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}}, \phi = \tan^{-1} \frac{\omega L}{R}, \tau = \frac{L}{R}$$

過渡電流の大きさ  $\propto \sin(\theta - \phi)$

$$\theta - \phi = 0, \pi \longrightarrow \text{過渡電流 } 0$$

$$\theta - \phi = \pm \frac{\pi}{2} \longrightarrow \text{過渡電流最大}$$

$$\theta - \phi = 0$$

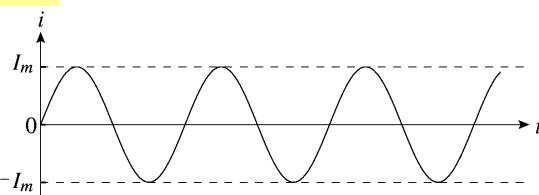

$$\theta - \phi = \frac{\pi}{2}$$



#### ・RC直列回路

$$\text{電源電圧 } v(t) = V_m \sin(\omega t + \theta)$$

回路方程式

$$Ri + \frac{q}{C} = V_m \sin(\omega t + \theta) \longrightarrow i = \frac{dq}{dt}$$

$$q = q_t + q_s$$

・定常解

$$j\omega R Q_s + \frac{Q_s}{C} = V_e e^{j\theta} \longrightarrow Q_s = \frac{CV_e e^{j\theta}}{1 + j\omega CR} = \frac{CV_e}{\sqrt{1 + \omega^2 C^2 R^2}} e^{j(\theta - \phi)}$$


$\left( V_e = \frac{V_m}{\sqrt{2}}, \phi = \tan^{-1} \omega CR \right)$

よって

$$q_s = Q_m \sin(\omega t + \theta - \phi) \quad \left( Q_m = \frac{V_m}{\sqrt{1 + \omega^2 C^2 R^2}} \right)$$

・過渡解
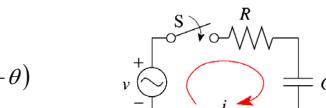
$$R \frac{dq_t}{dt} + \frac{q_t}{C} = 0 \longrightarrow q_t = A e^{-t/\tau} \quad (\text{時定数 } \tau = CR)$$



一般解

$$q = q_i + q_s = Ae^{-t/\tau} + Q_m \sin(\omega t + \theta - \phi)$$

初期条件  $t=0 \Leftrightarrow q=0$

$$A + Q_m \sin(\theta - \phi) = 0 \rightarrow A = -Q_m \sin(\theta - \phi)$$

よって

$$q = Q_m \sin(\omega t + \theta - \phi) - Q_m \sin(\theta - \phi)e^{-t/\tau}$$

$$\text{ただし } Q_m = \frac{CV_m}{\sqrt{1+\omega^2 C^2 R^2}}, \quad \phi = \tan^{-1} \omega CR, \quad \tau = CR$$

$$\begin{aligned} i &= \frac{dq}{dt} = \omega Q_m \cos(\omega t + \theta - \phi) + \frac{Q_m}{\tau} \sin(\theta - \phi)e^{-t/\tau} \\ &= I_m \left\{ \cos(\omega t + \theta - \phi) + \cot \phi \sin(\theta - \phi)e^{-t/\tau} \right\} \end{aligned}$$

$$\text{ただし } I_m = \frac{\omega CV_m}{\sqrt{1+\omega^2 C^2 R^2}}, \quad \phi = \tan^{-1} \omega CR, \quad \tau = CR$$

教科書演習問題問6との関係

$$\tilde{\phi} = \tan^{-1} \frac{1}{\omega CR} \text{ と置くと}$$

$$\cot \phi = \frac{1}{\tan \phi} = \frac{1}{\omega CR} = \tan \tilde{\phi}$$

$$\theta - \phi = \theta - \left( \frac{\pi}{2} - \tilde{\phi} \right) = \theta + \tilde{\phi} - \frac{\pi}{2}$$

$$\sin(\theta - \phi) = \sin \left( \theta + \tilde{\phi} - \frac{\pi}{2} \right) = -\cos(\theta + \tilde{\phi})$$

$$\cos(\omega t + \theta - \phi) = \cos \left( \omega t + \theta + \tilde{\phi} - \frac{\pi}{2} \right) = \sin(\omega t + \theta + \tilde{\phi})$$



$$i = I_m \left\{ \sin(\omega t + \theta + \tilde{\phi}) - \tan \tilde{\phi} \cos(\theta + \tilde{\phi})e^{-t/\tau} \right\}$$

### 方形パルス入力に対する応答

RC直列回路の過渡現象の一般解

$$q = Ae^{-t/\tau} + CE_s$$

$t = t_0 \Leftrightarrow q = q_0$

$$q = CE_s + (q_0 - CE_s)e^{-(t-t_0)/\tau}$$

$$t < 0$$



$$q = 0$$

$$0 \leq t < T$$

$$q = CE - CEe^{-t/\tau} = CE(1 - e^{-t/\tau})$$

$$t > T$$
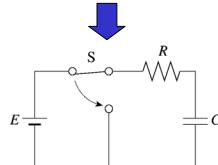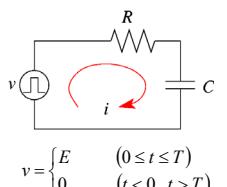
$$q = q(T)e^{-(t-T)/\tau} = CE(1 - e^{-T/\tau})e^{-(t-T)/\tau}$$



### 微分回路

• RL 直列回路において

$$v_L = L \frac{di}{dt} = L \frac{dv_R}{dt} \quad \frac{\tau = L/R \ll T}{v_R \cong v} \rightarrow v_L \cong \frac{L}{R} dv$$

(電源電圧の微分に比例)

• RC 直列回路において

$$v_R = Ri = R \frac{dq}{dt} = CR \frac{dv_C}{dt} \quad \frac{\tau = CR \ll T}{v_C \cong v} \rightarrow v_R \cong CR \frac{dv}{dt}$$

### 積分回路

• RC 直列回路において

$$v_C = \frac{q}{C} = \frac{1}{C} \int idt = \frac{1}{CR} \int v_R dt \quad \frac{\tau = L/R \gg T}{v_R \cong v} \rightarrow v_C = \frac{1}{CR} \int v dt$$

(電源電圧の積分に比例)

• RL 直列回路において

$$v_R = Ri = \frac{R}{L} \int v_L dt \quad \frac{\tau = L/R \gg T}{v_L \cong v} \rightarrow v_R \cong \frac{R}{L} \int v dt$$