

理想変成器

結合係数 $k=1$
励磁インダクタンス $L_1, L_2 \rightarrow \infty$


(電圧比は巻数比に等しい)

$$V_1 = \pm \frac{N_1}{N_2} V_2$$

$$I_1 = \pm \frac{N_2}{N_1} I_2 \rightarrow V_1 I_1 = V_2 I_2 \text{ (無損失)}$$

(電流比は巻数比の逆数に等しい)

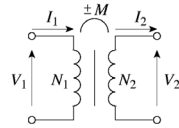
$$Z_i = \left(\frac{N_1}{N_2}\right)^2 Z_L \text{ (インピーダンスは巻数比の2乗で変換される)}$$



電流の向きに注意

通常は巻数比で表記

$$n = \frac{N_2}{N_1}$$

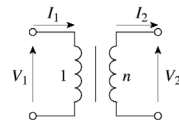

(例)

$$n = 10, R = 5\Omega, V_1 = 3V$$

$$V_2 = nV_1 = 10 \times 3 = 30V$$


$$I_2 = \frac{V_2}{R} = \frac{30}{5} = 6A$$

$$I_1 = nI_2 = 10 \times 6 = 60A$$

$$I_1, I_2, V_2?$$

↓

(別解)

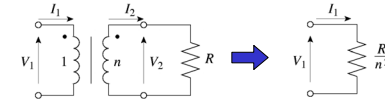

$$I_1 = \frac{V_1}{R/n^2} = \frac{3}{5/100} = 60A$$

$$\begin{cases} V_2 = nV_1 = 10 \times 3 = 30V \\ I_2 = \frac{I_1}{n} = \frac{60}{10} = 6A \end{cases}$$

理想変成器の関係式の導出

$$\begin{cases} V_1 = j\omega L_1 I_1 \mp j\omega M I_2 \\ V_2 = \pm j\omega M I_1 - j\omega L_2 I_2 \end{cases} \xrightarrow{\text{代入}} I_1 = \pm \frac{1}{j\omega M} V_2 \pm \frac{L_2}{M} I_2$$


$$\begin{cases} V_1 = \pm \frac{L_1}{M} V_2 \pm j\omega \left(\frac{L_1 L_2}{M} - M\right) I_2 = \pm \frac{L_1}{M} V_2 \pm j\omega \left(\frac{L_1 L_2 (1-k^2)}{M}\right) I_2 \\ I_1 = \pm \frac{1}{j\omega M} V_2 \pm \frac{L_2}{M} I_2 \end{cases}$$

$$k=1 \quad (M = \sqrt{L_1 L_2})$$

$$L_1, L_2 \rightarrow \infty \quad (M \rightarrow \infty)$$

$$\begin{cases} V_1 = \pm \sqrt{\frac{L_1}{L_2}} V_2 \\ I_1 = \pm \sqrt{\frac{L_2}{L_1}} I_2 \end{cases} \xrightarrow{L_1 \propto N_1^2, L_2 \propto N_2^2} \begin{cases} V_1 = \pm \frac{N_1}{N_2} V_2 \text{ (電圧比は巻数比に等しい)} \\ I_1 = \pm \frac{N_2}{N_1} I_2 \text{ (電流比は巻数比の逆数に等しい)} \end{cases}$$

一般の変成器の理想変成器による表現

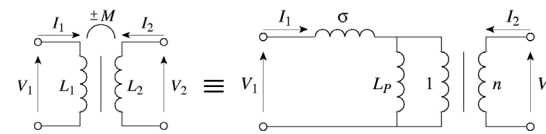

二次側短絡

$$V_1 = j\omega \frac{L_1 L_2 - M^2}{L_2} I_1 \quad V_1 = j\omega \sigma I_1 \quad \Rightarrow \quad \sigma = \frac{L_1 L_2 + M^2}{L_2} = L_1 (1-k^2)$$

二次側開放

$$V_1 = j\omega L_1 I_1 \quad V_1 = j\omega (\sigma + L_p) I_1 \quad \Rightarrow \quad L_p = L_1 - \sigma = k^2 L_1$$

一次側開放

$$V_2 = j\omega L_2 I_2 \quad V_2 = j\omega (n^2 L_p) I_2 \quad \Rightarrow \quad n = \sqrt{\frac{L_2}{L_p}} = \frac{1}{k} \sqrt{\frac{L_2}{L_1}}$$